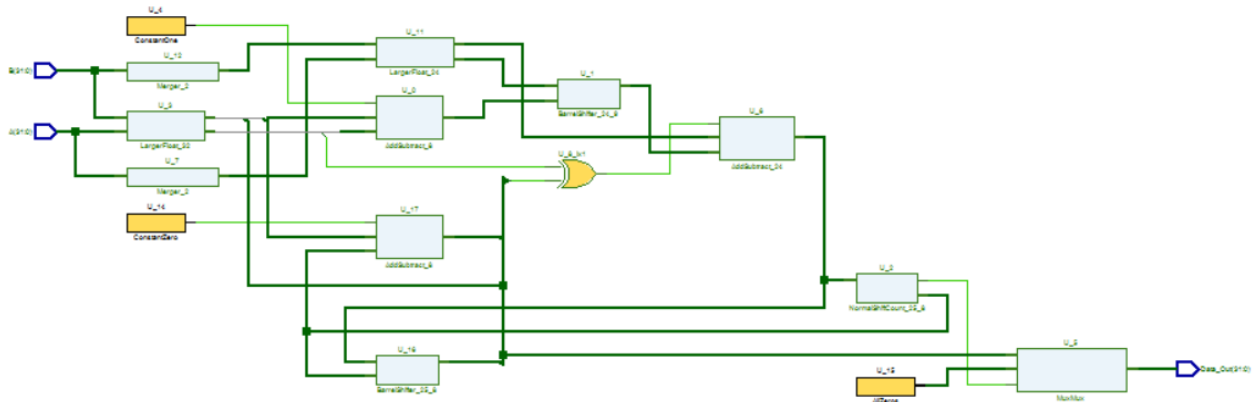


## Combinational Floating Point Adder

Schematic:



Resource Requirements:


```

*****
Device Utilization for 10M08DAF256C7G
*****
Resource                                Used    Avail    Utilization
-----
IOs                                     96      178      53.93%
LUTs                                   1359    8064      16.85%
Registers                              0      8064       0.00%
Memory Bits                            0    387072     0.00%
DSP block 9-bit elems                   0       48       0.00%
  
```

There are no registers utilization for the FPGA requirement report for the combinational datapath.

## Sequential Floating Point Data Path

*Schematic:*

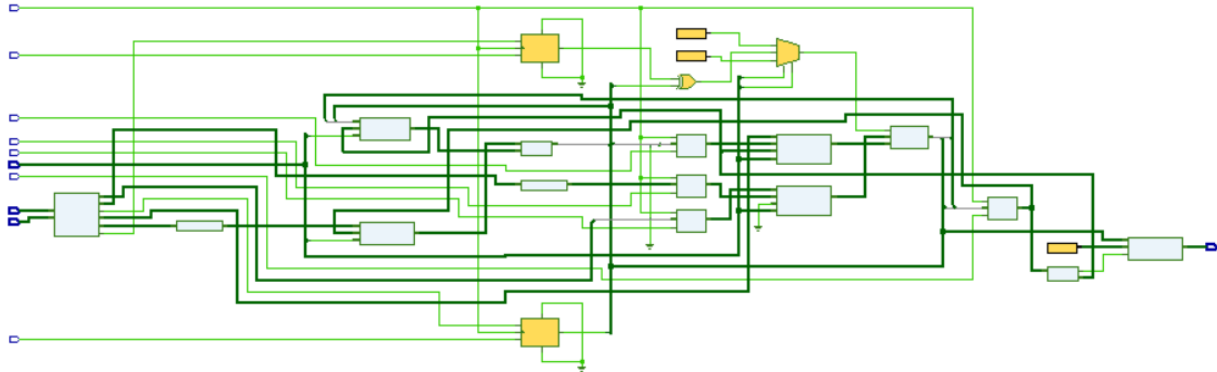

There are a lot of more wires associated with this design. It looks like the RTL made some of the MUXs boxes for some reason.


*Resource Requirements:*

```
*****
Device Utilization for 10M08DAF256C7G
*****
```

Resource	Used	Avail	Utilization
IOs	105	178	58.99%
LUTs	999	8064	12.39%
Registers	83	8064	1.03%
Memory Bits	0	387072	0.00%
DSP block 9-bit elems	0	48	0.00%

There are now registers utilization now for the FPGA device.


## Sequential Control Unit

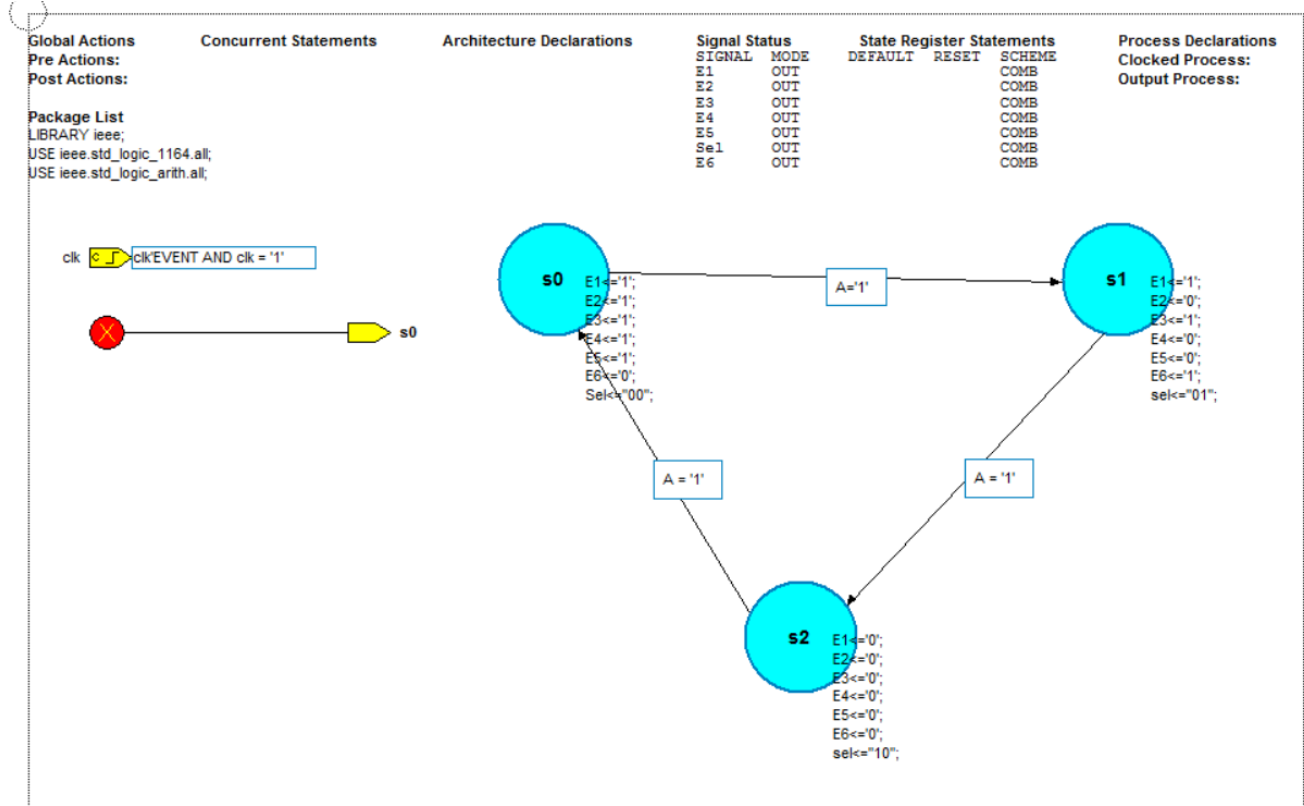

The FSM machine controls the enables on the registers to determine when the store and when to not store; these are my E's. The Sel variable is the selector for the MUXs. The Sel variable changes depending on the clock cycle. It goes to "00" to "01" to "10" to indicate the cycle.

## Sequential Floating Point Adder (Data Path + Control Unit)

Schematic:

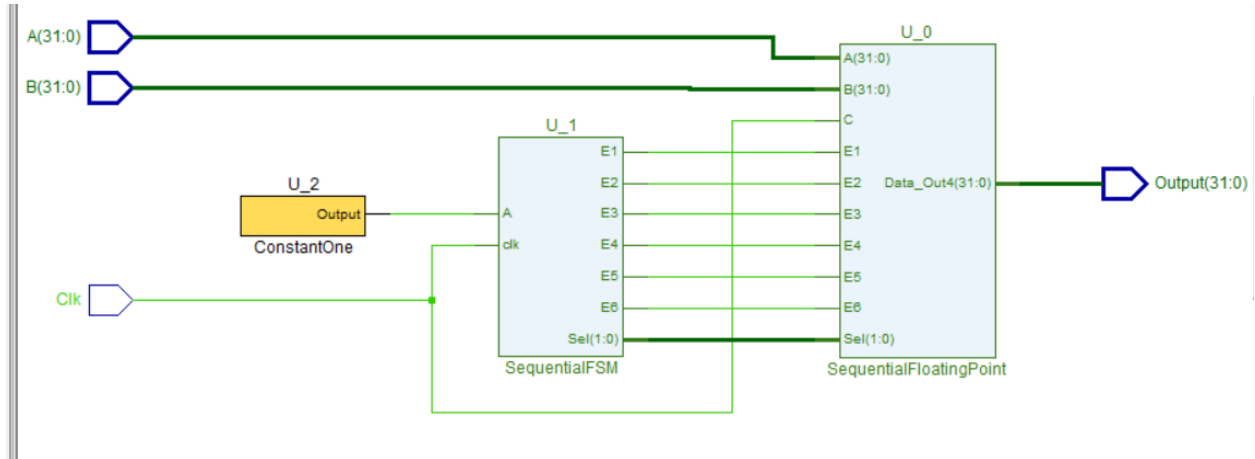

This schematic connects the FSM with the Sequential Datapath.

Resource Requirements:

```
*****
Device Utilization for 10M08DAF256C7G
*****
```

Resource	Used	Avail	Utilization
IOs	97	178	54.49%
LUTs	1000	8064	12.40%
Registers	85	8064	1.05%
Memory Bits	0	387072	0.00%
DSP block 9-bit elems	0	48	0.00%

```
-----
```

Registers are now being used for the FPGA utilization.

## Sequential TestBench

```

10  LIBRARY ieee;
11  USE ieee.std_logic_1164.all;
12  use ieee.numeric_std.all;
13
14  ENTITY SequentialTestBench IS
15  END ENTITY SequentialTestBench;
16
17  --
18  ARCHITECTURE Behavior OF SequentialTestBench IS
19      SIGNAL clock : std_logic;
20      Signal A, B, Output: std_logic_vector(31 DOWNT0 0);
21  BEGIN
22      DUT: ENTITY work.SequentialProcessFlow(Struct)
23          PORT MAP(A=>A, B=>B, Output=>Output, clk=>clock);
24      PROCESS
25          BEGIN
26              clock <= '1';
27              WAIT FOR 50 ns;
28              clock <= '0';
29              WAIT FOR 50 ns;
30          END PROCESS;
31      PROCESS
32          BEGIN
33              A<="0100000001010000000000000000000000";
34              B<="0100000001110000000000000000000000";
35              WAIT FOR 500 ns; --Some kind of slew start affected the initial result
36              WAIT FOR 250 ns; -- Check the value in-between the 3rd state
37              assert (Output = "01000001010000000000000000000000")
38                  report "Test 1 Failure";
39              WAIT FOR 50 ns;
40

```

```

41      A<="0100000010011000000000000000000000";
42      B<="0100000010001100000000000000000000";
43      WAIT FOR 300 ns;
44      WAIT FOR 250 ns;
45      assert (Output = "01000000110011000000000000000000")
46          report "Test 2 Failure";
47      WAIT FOR 50 ns;
48
49      A<="010000001111110000000000000000000000";
50      B<="110000001011100000000000000000000000";
51      WAIT FOR 300 ns;
52      WAIT FOR 250 ns;
53      assert (Output = "0100000011000000000000000000000000")
54          report "Test 3 Failure";
55      WAIT FOR 50 ns;
56
57      A<="11000000111100101100110011001101010";
58      B<="0100000010101010101100110011001101010";
59      WAIT FOR 250 ns;
60      assert (Output = "1100000010111010110011001100110101")
61          report "Test 4 Failure";
62      WAIT FOR 50 ns;
63
64      A<="010000001001100000000000000000000000";
65      B<="000000000000000000000000000000000000";
66      WAIT FOR 250 ns;
67      assert (Output = "0100000010011000000000000000000000")
68          report "Test 5 Failure";
69      WAIT FOR 50 ns;
70      WAIT;
71  END PROCESS;
72  END ARCHITECTURE Behavior;

```

Testbench worked out well. I made the program report a test failure if there was a problem. I tested 5 different cases. Two different cases for adding two positive floating numbers, two different cases for adding two negative floating point numbers, one adding a negative and positive floating point numbers, and finally one adding a positive floating point number with a 0. I extend WAIT to 500 initially due to some clock skew delay for some reason that causes the first input entry not to register immediately. Within the cases, I extended to 6 clock cycles just in case the new immediate input entries does not register for the 1<sup>st</sup> 3 clock cycles. But the correct value is definitely given at the end of the 2<sup>nd</sup> 3 clock cycles. Also, I asserted within the middle of 3<sup>rd</sup> cycle and not towards the falling edge of the 3<sup>rd</sup> clock cycle to avoid any output changes when the input changes.